

Index Number: \_\_\_\_\_ Programme: \_\_\_\_\_



UNIVERSITY OF ENERGY AND NATURAL RESOURCES, SUNYANI, GHANA  
SCHOOL OF ENGINEERING

DEPARTMENT OF COMPUTER AND ELECTRICAL ENGINEERING

LEVEL 200: MID-SEMESTER EXAMINATION- 2018/2019

Bachelor of Science (Comp/ Renewable /Electrical Engineering)

CENG 102: ELECTRICAL CIRCUIT DESIGN


May, 2018

Total Time: 1:45 Hours

Part 1: Solve all the questions in this section

1. Find the current  $I_1$ ,  $I_2$  and  $I_3$  in the circuit in Figure 1.

*W/ 4 + 5*

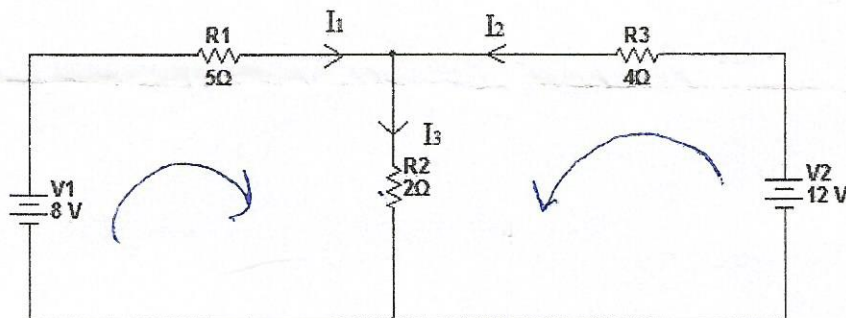

*✓  
(8A, -4A, 14A)*

$$8 = 5I_1 + 2I_3$$

$$12 = 4I_2 + 2I_3$$

but  $I_3 = I_1 + I_2$  Find the current  $i$  in the Circuit in Figure 2.


$$12 = 4I_2 + 2(I_1 + I_2)$$

$$12 = 4I_2 + 2I_1 + 2I_2$$

$$8 = 5I_1 + 2(I_1 + I_2)$$

$$8 = 5I_1 + 2I_1 + 2I_2$$

$$8 = 7I_1 + 2I_2$$

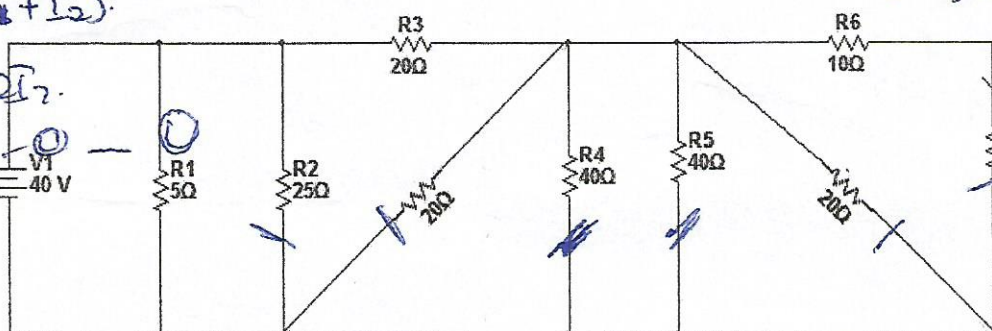

$$12 = 6I_2 + 2I_1$$

$$12 = 2I_1 + 6I_2$$

$$6 = I_1 + 3I_2$$

*12*

*8.33 A. 8.33.*

Index Number: \_\_\_\_\_ Programme: \_\_\_\_\_


3.

(a) Find the Thevenin equivalent circuit across the variable load resistor,  $R_L$  in Figure 3

(b) Find the current through  $R_L$  when

- i.  $R_L = 5 \Omega$
- ii.  $R_L = 7 \Omega$
- iii.  $R_L = 12 \Omega$

(c) Find the maximum power through  $R_L$ .

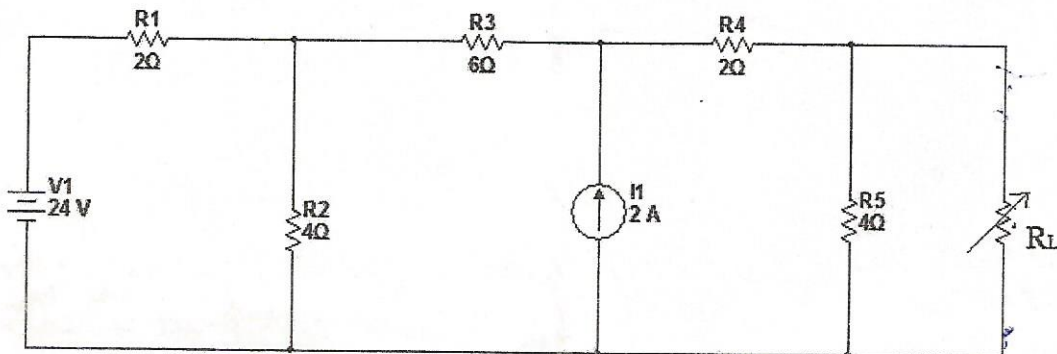

Part 2: Solve all the questions in this section

1.

- i. Briefly explain two factors that cause capacitors to deviate from their ideal characteristics
- ii. Briefly explain using graph, the transient charging and discharging of a capacity
- iii. State three application of the capacitor

*Answer for 1.1*

*Answer - 2.*

- i. How is the inductance related to the magnetic field?
- ii. Briefly explain using graph, the transient storing and release of a inductor
- iii. State three application of the inductor

*Answer -*



DEPARTMENT OF COMPUTER AND ELECTRICAL ENGINEERING  
CENG 201:ELECTRICAL CIRCUIT DESIGN-QUIZ

NOV, 2017

Duration: 45 minutes

Instruction(s): Answer All Questions

1. Find  $v_2/v_1$  in the circuit shown in Figure 1

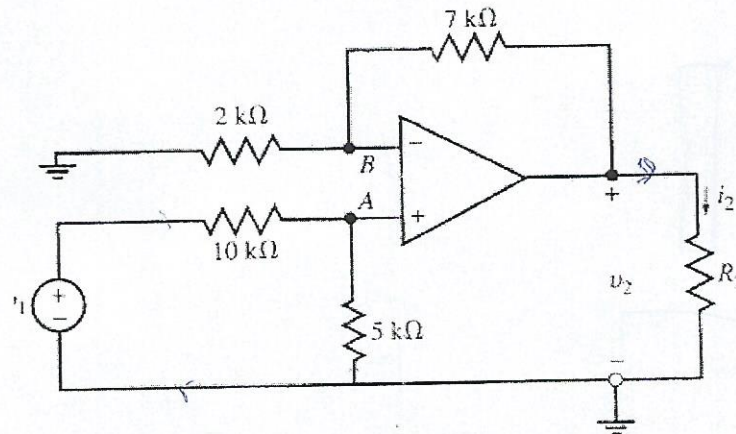


Figure 1: For Question 1

2. Find Thevenin equivalent of the circuit of 2 seen from terminals AB

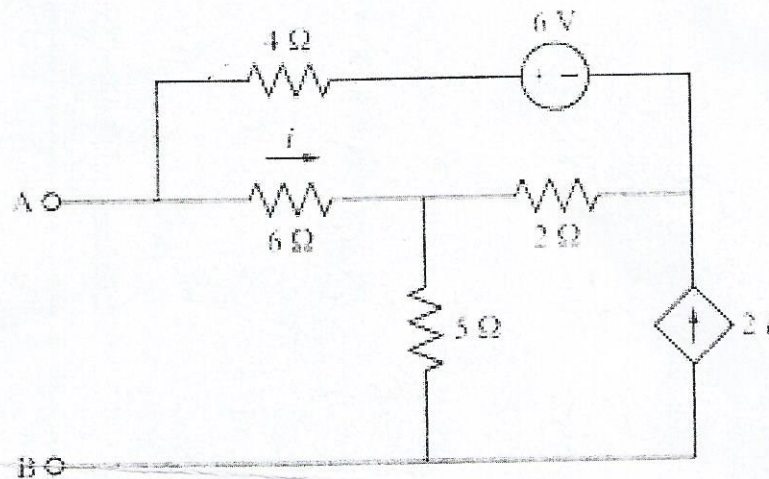


Figure 2: For Question 2

677

 $T_1 = \frac{21}{40}$

Index Number: \_\_\_\_\_ Programme: \_\_\_\_\_



UNIVERSITY OF ENERGY AND NATURAL RESOURCES, SUNYANI, GHANA  
SCHOOL OF ENGINEERING

DEPARTMENT OF COMPUTER AND ELECTRICAL ENGINEERING

LEVEL 200: MID-SEMESTER EXAMINATION- 2018/2019

Bachelor of Science (Comp/ Renewable /Electrical Engineering)

CENG 102: ELECTRICAL CIRCUIT DESIGN


May, 2018

Total Time: 1:45 Hours

**Part 1: Solve all the questions in this section**

1. Find the current  $I_1$ ,  $I_2$  and  $I_3$  in the circuit in Figure 1.

*w/ 4 + 5*

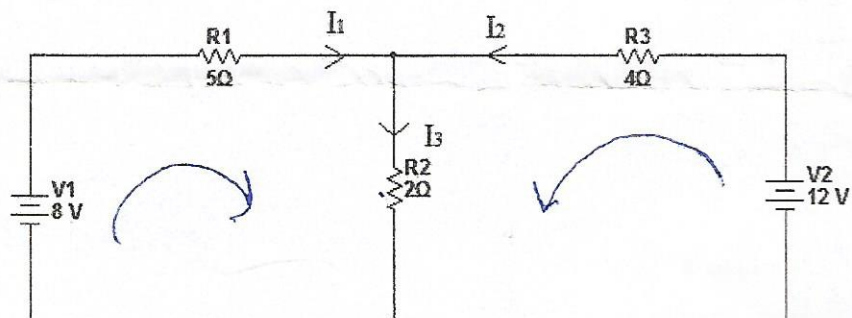

*✓  
(8A, -4A, 1A)*

$$8 = 5I_1 + 2I_2$$

but  $I_3 = I_2 + I_1$  Find the current  $i$  in the Circuit in Figure 2.

$$8 = 5I_1 + 2(I_1 + I_2)$$

$$8 = 5I_1 + 2I_1 + 2I_2$$

$$8 = 7I_1 + 2I_2$$

$$12 = 4I_2 + 2I_3$$

$$12 = 4I_2 + 2(I_1 + I_2)$$

$$12 = 4I_2 + 2I_1 + 2I_2$$

$$12 = 6I_2 + 2I_1$$

$$12 = 2I_1 + 6I_2$$


$$6 = I_1 + 3I_2$$

$$6 = I_1 + 3I_2$$

$$6 = I_1 + 3I_2$$

$$6 = I_1 + 3I_2$$

$$6 = I_1 + 3I_2$$

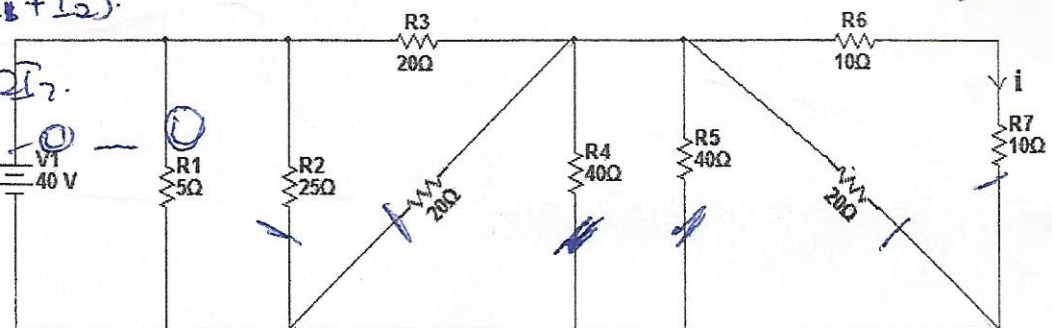

*B: 33 n. 8-33.*



Index Number: \_\_\_\_\_ Programme: \_\_\_\_\_


3.

(a) Find the Thevenin equivalent circuit across the variable load resistor,  $R_L$  in Figure 3

(b) Find the current through  $R_L$  when

- i.  $R_L = 5 \Omega$
- ii.  $R_L = 7 \Omega$
- iii.  $R_L = 12 \Omega$

(c) Find the maximum power through  $R_L$ .

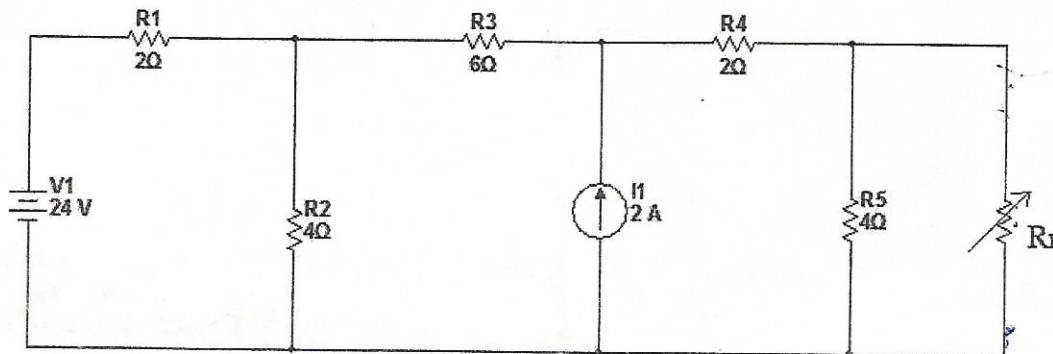

**Part 2: Solve all the questions in this section**

1.

- i. Briefly explain two factors that cause capacitors to deviate from their ideal characteristics
- ii. Briefly explain using graph, the transient charging and discharging of a capacity
- iii. State three application of the capacitor

Area - 2.

- i. How is the inductance related to the magnetic field?
- ii. Briefly explain using graph, the transient storing and release of a inductor
- iii. State three application of the inductor

distu -

Amag F/L turn